

HW 2: 1.28, and 2.1 through 2.8 due 20 January

Problem 1.28 A series RLC circuit is connected to a generator with a voltage $v_s(t) = V_0 \cos(\omega t + \pi/3)$ (V).

- (a) Write the voltage loop equation in terms of the current $i(t)$, R , L , C , and $v_s(t)$.
- (b) Obtain the corresponding phasor-domain equation.
- (c) Solve the equation to obtain an expression for the phasor current \tilde{I} .

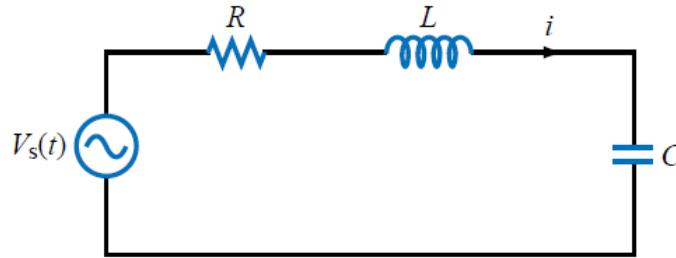


Figure P1.28: RLC circuit.

Solution:

(a) $v_s(t) = Ri + L \frac{di}{dt} + \frac{1}{C} \int i dt.$

(b) In phasor domain: $\tilde{V}_s = R\tilde{I} + j\omega L\tilde{I} + \frac{\tilde{I}}{j\omega C}.$

(c) $\tilde{I} = \frac{\tilde{V}_s}{R + j(\omega L - 1/\omega C)} = \frac{V_0 e^{j\pi/3}}{R + j(\omega L - 1/\omega C)} = \frac{\omega C V_0 e^{j\pi/3}}{\omega RC + j(\omega^2 LC - 1)}.$

Problem 2.1 A transmission line of length l connects a load to a sinusoidal voltage source with an oscillation frequency f . Assuming the velocity of wave propagation on the line is c , for which of the following situations is it reasonable to ignore the presence of the transmission line in the solution of the circuit:

- (a) $l = 20 \text{ cm}$, $f = 20 \text{ kHz}$,
- (b) $l = 50 \text{ km}$, $f = 60 \text{ Hz}$,
- (c) $l = 20 \text{ cm}$, $f = 600 \text{ MHz}$,
- (d) $l = 1 \text{ mm}$, $f = 100 \text{ GHz}$.

Solution: A transmission line is negligible when $l/\lambda \leq 0.01$.

- (a) $\frac{l}{\lambda} = \frac{lf}{u_p} = \frac{(20 \times 10^{-2} \text{ m}) \times (20 \times 10^3 \text{ Hz})}{3 \times 10^8 \text{ m/s}} = 1.33 \times 10^{-5} \text{ (negligible).}$
 - (b) $\frac{l}{\lambda} = \frac{lf}{u_p} = \frac{(50 \times 10^3 \text{ m}) \times (60 \times 10^0 \text{ Hz})}{3 \times 10^8 \text{ m/s}} = 0.01 \text{ (borderline).}$
 - (c) $\frac{l}{\lambda} = \frac{lf}{u_p} = \frac{(20 \times 10^{-2} \text{ m}) \times (600 \times 10^6 \text{ Hz})}{3 \times 10^8 \text{ m/s}} = 0.40 \text{ (nonnegligible).}$
 - (d) $\frac{l}{\lambda} = \frac{lf}{u_p} = \frac{(1 \times 10^{-3} \text{ m}) \times (100 \times 10^9 \text{ Hz})}{3 \times 10^8 \text{ m/s}} = 0.33 \text{ (nonnegligible).}$
-

Problem 2.2 A two-wire copper transmission line is embedded in a dielectric material with $\epsilon_r = 2.6$ and $\sigma = 2 \times 10^{-6}$ S/m. Its wires are separated by 3 cm and their radii are 1 mm each.

- (a) Calculate the line parameters R' , L' , G' , and C' at 2 GHz.
- (b) Compare your results with those based on CD Module 2.1. Include a printout of the screen display.

Solution:

- (a) Given:

$$\begin{aligned}
 f &= 2 \times 10^9 \text{ Hz}, \\
 d &= 2 \times 10^{-3} \text{ m}, \\
 D &= 3 \times 10^{-2} \text{ m}, \\
 \sigma_c &= 5.8 \times 10^7 \text{ S/m (copper)}, \\
 \epsilon_r &= 2.6, \\
 \sigma &= 2 \times 10^{-6} \text{ S/m}, \\
 \mu &= \mu_c = \mu_0.
 \end{aligned}$$


From Table 2-1:

$$\begin{aligned}
 R_s &= \sqrt{\pi f \mu_c / \sigma_c} \\
 &= [\pi \times 2 \times 10^9 \times 4\pi \times 10^{-7} / 5.8 \times 10^7]^{1/2} \\
 &= 1.17 \times 10^{-2} \Omega, \\
 R' &= \frac{2R_s}{\pi d} = \frac{2 \times 1.17 \times 10^{-2}}{2\pi \times 10^{-3}} = 3.71 \Omega/\text{m}, \\
 L' &= \frac{\mu}{\pi} \ln \left[(D/d) + \sqrt{(D/d)^2 - 1} \right] \\
 &= 1.36 \times 10^{-6} \text{ H/m}, \\
 G' &= \frac{\pi \sigma}{\ln[(D/d) + \sqrt{(D/d)^2 - 1}]} \\
 &= 1.85 \times 10^{-6} \text{ S/m}, \\
 C' &= \frac{G' \epsilon}{\sigma} \\
 &= \frac{1.85 \times 10^{-6} \times 8.85 \times 10^{-12} \times 2.6}{2 \times 10^{-6}} \\
 &= 2.13 \times 10^{-11} \text{ F/m}.
 \end{aligned}$$

- (b) Solution via Module 2.1:


Module 2.1 Two-Wire Line

Select: Impedance vs. Distance D

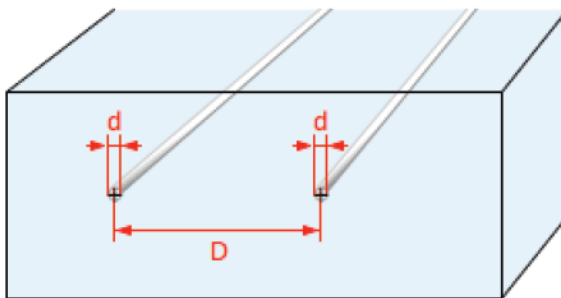

Substrate
 $\epsilon_r = 2.6$
 $\sigma = 2.0E-6$ [S/m]

Wires
 $\sigma_c = 5.8E7$ [S/m]

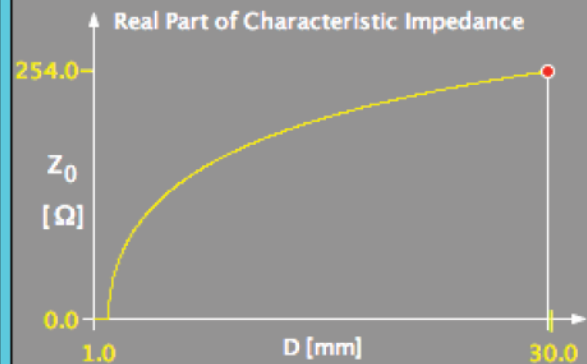

Input

Wire Diameter $d = 2.0$ [mm]

Range

Centers distance $D = 30.0$ [mm]

Range

Frequency $f = 2.0E9$ [Hz]

Range

ϵ_r σ [S/m] σ_c [S/m]
 2.6 2E-6 5.8E7

Update

Output

$f = 2.0$ [GHz]

Structure Data

$d = 2.0$ [mm] $D / d = 15.0$
 $D = 30.0$ [mm]

$Z_0 = 253.037142 - j 0.026617$ [Ω]

$C' = 21.241303$ [pF/m]

$L' = 1.360034$ [μH/m]

$R' = 3.713907$ [Ω/m]

$G' = 2.0E-6$ [S/m]

$\lambda_0 = 0.15$ [m] in vacuum

$\lambda = 9.3026$ [cm] in guide

$\alpha = 0.007572$ [Np/m]

$\beta = 67.542213$ [rad/m]

Problem 2.3 Show that the transmission line model shown in Fig. P2.3 yields the same telegrapher's equations given by Eqs. (2.14) and (2.16).

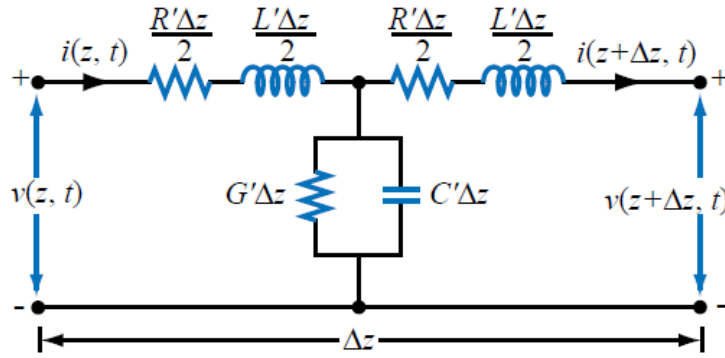


Figure P2.3: Transmission line model.

Solution: The voltage at the central upper node is the same whether it is calculated from the left port or the right port:

$$\begin{aligned} v(z + \tfrac{1}{2}\Delta z, t) &= v(z, t) - \tfrac{1}{2}R'\Delta z i(z, t) - \tfrac{1}{2}L'\Delta z \frac{\partial}{\partial t} i(z, t) \\ &= v(z + \Delta z, t) + \tfrac{1}{2}R'\Delta z i(z + \Delta z, t) + \tfrac{1}{2}L'\Delta z \frac{\partial}{\partial t} i(z + \Delta z, t). \end{aligned}$$

Recognizing that the current through the $G' \parallel C'$ branch is $i(z, t) - i(z + \Delta z, t)$ (from Kirchhoff's current law), we can conclude that

$$i(z, t) - i(z + \Delta z, t) = G'\Delta z v(z + \tfrac{1}{2}\Delta z, t) + C'\Delta z \frac{\partial}{\partial t} v(z + \tfrac{1}{2}\Delta z, t).$$

From both of these equations, the proof is completed by following the steps outlined in the text, ie. rearranging terms, dividing by Δz , and taking the limit as $\Delta z \rightarrow 0$.

Problem 2.4 A 1-GHz parallel-plate transmission line consists of 1.2-cm-wide copper strips separated by a 0.15-cm-thick layer of polystyrene. Appendix B gives $\mu_c = \mu_0 = 4\pi \times 10^{-7}$ (H/m) and $\sigma_c = 5.8 \times 10^7$ (S/m) for copper, and $\epsilon_r = 2.6$ for polystyrene. Use Table 2-1 to determine the line parameters of the transmission line. Assume $\mu = \mu_0$ and $\sigma \simeq 0$ for polystyrene.

Solution:

$$R' = \frac{2R_s}{w} = \frac{2}{w} \sqrt{\frac{\pi f \mu_c}{\sigma_c}} = \frac{2}{1.2 \times 10^{-2}} \left(\frac{\pi \times 10^9 \times 4\pi \times 10^{-7}}{5.8 \times 10^7} \right)^{1/2} = 1.38 \quad (\Omega/\text{m}),$$

$$L' = \frac{\mu d}{w} = \frac{4\pi \times 10^{-7} \times 1.5 \times 10^{-3}}{1.2 \times 10^{-2}} = 1.57 \times 10^{-7} \quad (\text{H/m}),$$

$$G' = 0 \quad \text{because } \sigma = 0,$$

$$C' = \frac{\epsilon w}{d} = \epsilon_0 \epsilon_r \frac{w}{d} = \frac{10^{-9}}{36\pi} \times 2.6 \times \frac{1.2 \times 10^{-2}}{1.5 \times 10^{-3}} = 1.84 \times 10^{-10} \quad (\text{F/m}).$$

Problem 2.5 For a parallel-plate transmission line, the line parameters are given by:

$$\begin{aligned}R' &= 1 \quad (\Omega/\text{m}), \\L' &= 167 \quad (\text{nH}/\text{m}), \\G' &= 0, \\C' &= 172 \quad (\text{pF}/\text{m}).\end{aligned}$$

Find α , β , u_p , and Z_0 at 1 GHz.

Solution: At 1 GHz, $\omega = 2\pi f = 2\pi \times 10^9$ rad/s. Application of (2.22) gives:

$$\begin{aligned}\gamma &= \sqrt{(R' + j\omega L')(G' + j\omega C')} \\&= [(1 + j2\pi \times 10^9 \times 167 \times 10^{-9})(0 + j2\pi \times 10^9 \times 172 \times 10^{-12})]^{1/2} \\&= [(1 + j1049)(j1.1)]^{1/2} \\&= \left[\sqrt{1 + (1049)^2} e^{j \tan^{-1} 1049} \times 1.1 e^{j90^\circ} \right]^{1/2}, \quad (j = e^{j90^\circ}) \\&= \left[1049 e^{j89.95^\circ} \times 1.1 e^{j90^\circ} \right]^{1/2} \\&= \left[1154 e^{j179.95^\circ} \right]^{1/2} \\&= 34 e^{j89.97^\circ} = 34 \cos 89.97^\circ + j34 \sin 89.97^\circ = 0.016 + j34.\end{aligned}$$

Hence,

$$\begin{aligned}\alpha &= 0.016 \text{ Np/m}, \\ \beta &= 34 \text{ rad/m}.\end{aligned}$$

$$\begin{aligned}u_p &= \frac{\omega}{\beta} = \frac{2\pi f}{\beta} = \frac{2\pi \times 10^9}{34} = 1.85 \times 10^8 \text{ m/s} \\Z_0 &= \left[\frac{R' + j\omega L'}{G' + j\omega C'} \right]^{1/2} \\&= \left[\frac{1049 e^{j89.95^\circ}}{1.1 e^{j90^\circ}} \right]^{1/2} \\&= \left[954 e^{-j0.05^\circ} \right]^{1/2} \\&= 31 e^{-j0.025^\circ} \simeq (31 - j0.01) \Omega.\end{aligned}$$

Problem 2.6 A coaxial line with inner and outer conductor diameters of 0.5 cm and 1 cm, respectively, is filled with an insulating material with $\epsilon_r = 4.5$ and $\sigma = 10^{-3}$ S/m. The conductors are made of copper.

- (a) Calculate the line parameters at 1 GHz.
- (b) Compare your results with those based on CD Module 2.2. Include a printout of the screen display.

Solution: (a) Given

$$a = (0.5/2) \text{ cm} = 0.25 \times 10^{-2} \text{ m},$$

$$b = (1.0/2) \text{ cm} = 0.50 \times 10^{-2} \text{ m},$$

combining Eqs. (2.5) and (2.6) gives

$$\begin{aligned} R' &= \frac{1}{2\pi} \sqrt{\frac{\pi f \mu_c}{\sigma_c}} \left(\frac{1}{a} + \frac{1}{b} \right) \\ &= \frac{1}{2\pi} \sqrt{\frac{\pi(10^9 \text{ Hz})(4\pi \times 10^{-7} \text{ H/m})}{5.8 \times 10^7 \text{ S/m}}} \left(\frac{1}{0.25 \times 10^{-2} \text{ m}} + \frac{1}{0.50 \times 10^{-2} \text{ m}} \right) \\ &= 0.788 \text{ } \Omega/\text{m}. \end{aligned}$$

From Eq. (2.7),

$$L' = \frac{\mu}{2\pi} \ln \left(\frac{b}{a} \right) = \frac{4\pi \times 10^{-7} \text{ H/m}}{2\pi} \ln 2 = 139 \text{ nH/m}.$$

From Eq. (2.8),

$$G' = \frac{2\pi\sigma}{\ln(b/a)} = \frac{2\pi \times 10^{-3} \text{ S/m}}{\ln 2} = 9.1 \text{ mS/m}.$$

From Eq. (2.9),

$$C' = \frac{2\pi\epsilon}{\ln(b/a)} = \frac{2\pi\epsilon_r\epsilon_0}{\ln(b/a)} = \frac{2\pi \times 4.5 \times (8.854 \times 10^{-12} \text{ F/m})}{\ln 2} = 362 \text{ pF/m}.$$



(b) Solution via Module 2.2:

Module 2.2 Coaxial Cable

Select: Impedance vs. Radius b

$$\sigma = 0.0010 \text{ S/m}$$

$$\epsilon_r = 4.5$$

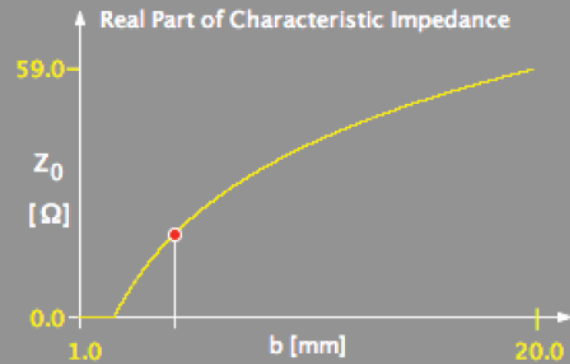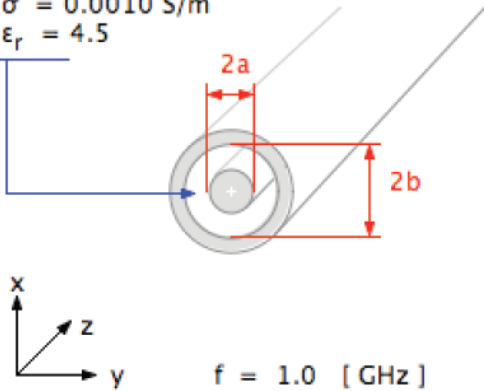

Input

Inner radius $a = 2.5$ [mm]

Range:

Shield radius $b = 5$ [mm]

Range:

Frequency $f = 1.0\text{E}9$ [Hz]

Range:

ϵ_r σ [S/m] σ_c [S/m]

4.5 1E-3 5.8E7

Update

Output

Structure Data

$a = 2.5$ [mm] $b / a = 2.0$

$b = 5.0$ [mm]

$Z_0 = 19.605065 + j 0.03034369$ [Ω]

$C' = 360.67376$ [pF/m]

$L' = 138.629436$ [nH/m]

$R' = 0.787839$ [Ω /m]

$G' = 0.009065$ [S/m]

$\lambda_0 = 0.3$ [m] in vacuum

$\lambda = 0.1414$ [m] in guide

$\alpha = 0.10895$ [Np/m]

$\beta = 44.428883$ [rad/m]

Problem 2.7 Find α , β , u_p , and Z_0 for the two-wire line of Problem 2.2. Compare results with those based on CD Module 2.1. Include a printout of the screen display.

Solution: From Problem 2.2:

$$R' = 3.71 \, \Omega/\text{m},$$

$$L' = 1.36 \times 10^{-6} \, \text{H/m},$$

$$G' = 1.85 \times 10^{-6} \, \text{S/m},$$

$$C' = 2.13 \times 10^{-11} \, \text{F/m}.$$

At 2 GHz:

$$\begin{aligned}\gamma &= \sqrt{(R' + j\omega L')(G' + j\omega C')} \\ &= 0.0076 + j67.54.\end{aligned}$$

Hence

$$\alpha = 0.0076 \, \text{Np/m},$$


$$\beta = 67.54 \, \text{rad/m}.$$

$$u_p = \frac{\omega}{\beta} = \frac{2\pi \times 2 \times 10^9}{67.54} = 1.86 \times 10^8 \, \text{m/s},$$

$$Z_0 = \sqrt{\frac{R' + j\omega L'}{G' + j\omega C'}} = 253 \, \Omega.$$


Module 2.1 Two-Wire Line

Select: Impedance vs. Distance D

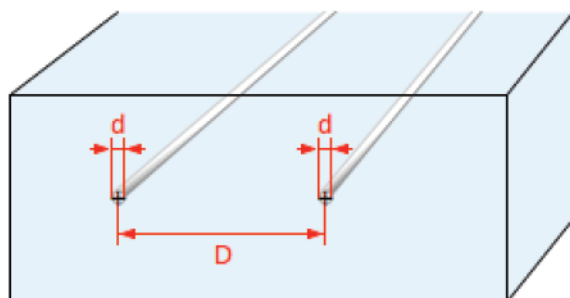

Substrate
 $\epsilon_r = 2.6$
 $\sigma = 2.0\text{E-}6$ [S/m]

Wires
 $\sigma_c = 5.8\text{E}7$ [S/m]

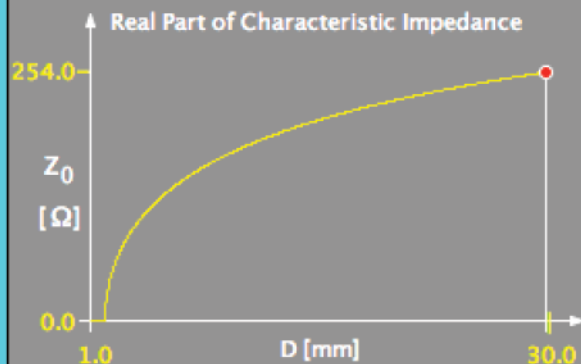

Input

Wire Diameter $d = 2.0$ [mm]

Range

Centers distance $D = 30.0$ [mm]

Range

Frequency $f = 2.0\text{E}9$ [Hz]

Range

ϵ_r σ [S/m] σ_c [S/m]

2.6 2E-6 5.8E7

Update

Output

$f = 2.0$ [GHz]

Structure Data

$d = 2.0$ [mm] $D / d = 15.0$
 $D = 30.0$ [mm]

$Z_0 = 253.037142 - j 0.026617$ [Ω]

$C' = 21.241303$ [pF/m]

$L' = 1.360034$ [μH/m]

$R' = 3.713907$ [Ω/m]

$G' = 2.0\text{E-}6$ [S/m]

$\lambda_0 = 0.15$ [m] in vacuum

$\lambda = 9.3026$ [cm] in guide

$\alpha = 0.007572$ [Np/m]

$\beta = 67.542213$ [rad/m]

Problem 2.8 Find α , β , u_p , and Z_0 for the coaxial line of Problem 2.6. Verify your results by applying CD Module 2.2. Include a printout of the screen display.

Solution: From Eq. (2.22),

$$\begin{aligned}\gamma &= \sqrt{(R' + j\omega L')(G' + j\omega C')} \\ &= \sqrt{(0.788 \, \Omega/\text{m}) + j(2\pi \times 10^9 \, \text{s}^{-1})(139 \times 10^{-9} \, \text{H/m})} \\ &\quad \times \sqrt{(9.1 \times 10^{-3} \, \text{S/m}) + j(2\pi \times 10^9 \, \text{s}^{-1})(362 \times 10^{-12} \, \text{F/m})} \\ &= (109 \times 10^{-3} + j44.5) \, \text{m}^{-1}.\end{aligned}$$

Thus, from Eqs. (2.25a) and (2.25b), $\alpha = 0.109 \, \text{Np/m}$ and $\beta = 44.5 \, \text{rad/m}$.

From Eq. (2.29),

$$\begin{aligned}Z_0 &= \sqrt{\frac{R' + j\omega L'}{G' + j\omega C'}} = \sqrt{\frac{(0.788 \, \Omega/\text{m}) + j(2\pi \times 10^9 \, \text{s}^{-1})(139 \times 10^{-9} \, \text{H/m})}{(9.1 \times 10^{-3} \, \text{S/m}) + j(2\pi \times 10^9 \, \text{s}^{-1})(362 \times 10^{-12} \, \text{F/m})}} \\ &= (19.6 + j0.030) \, \Omega.\end{aligned}$$

From Eq. (2.33),


$$u_p = \frac{\omega}{\beta} = \frac{2\pi \times 10^9}{44.5} = 1.41 \times 10^8 \, \text{m/s}.$$

Module 2.2 Coaxial Cable


Select: Impedance vs. Radius b

$$\sigma = 0.0010 \text{ S/m}$$

$$\epsilon_r = 4.5$$

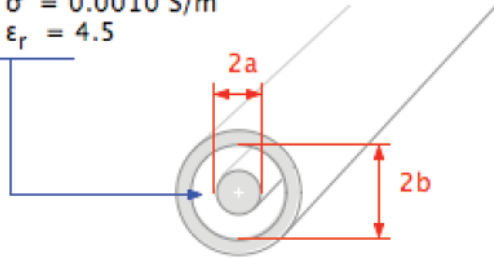

$$f = 1.0 \text{ [GHz]}$$

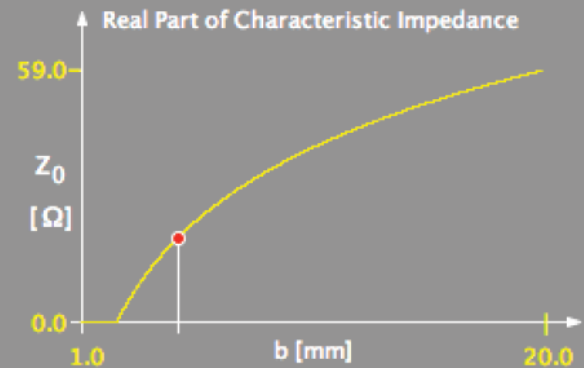

Input

Inner radius a = 2.5 [mm]

Range:

Shield radius b = 5 [mm]

Range:

Frequency f = 1.0E9 [Hz]

Range:

ϵ_r σ [S/m] σ_c [S/m]
4.5 1E-3 5.8E7

Update

Output

Structure Data

a = 2.5 [mm] b / a = 2.0
b = 5.0 [mm]

$Z_0 = 19.605065 + j 0.03034369 \text{ [} \Omega \text{]}$

$C' = 360.67376 \text{ [pF/m]}$

$L' = 138.629436 \text{ [nH/m]}$

$R' = 0.787839 \text{ [} \Omega \text{ /m]}$

$G' = 0.009065 \text{ [S/m]}$

$\lambda_0 = 0.3 \text{ [m]}$ in vacuum

$\lambda = 0.1414 \text{ [m]}$ in guide

$\alpha = 0.10895 \text{ [Np/m]}$

$\beta = 44.428883 \text{ [rad/m]}$